

$$1. R = R_1 + R_2 + R_3$$

$$R = 20 + 30 + 50$$

$$R = 100$$

$$2. I = 125 / 100$$

$$1.25A$$

$$3. I_1 = I_2 = I_3 = 1.25A$$

4. Ohm's law ($V = I * R$) for each individual resistor.

- **20 Ohm Resistor:**

$$V_1 = 1.25 * 20 = 25V$$

- **30 Ohm Resistor:**

$$V_2 = 1.25A * 30 = 37.5V$$

- **50 Ohm Resistor:**

$$V_3 = 1.25 A * 50 = 62.5V$$

5. Use Watt's law $P = V * I$

- **20:**

$$P_1 = 25 V * 1.25A = 31.25W$$

- **30:**

$$P_2 = 37.5V * 1.25A = 46.87 W$$

- **50:**

$$P_3 = 62.5V * 1.25 A = 78.125W$$

PART B

$$1. \quad 1/R = 1/R_1 + 1/R_2 + 1/R_3$$

$$1/R = 1/20 + 1/100 + 1/50$$

$$1/R = 8/100$$

$$R = 100/8$$

$$R = 12.5$$

$$2. \quad I = 125 / 12.5$$

$$10$$

$$3. \quad \text{Ohm's law } (I = V / R)$$

for each individual resistor.

20 Ohm Resistor:

$$I_1 = 125 / 20 = 6.25\text{A}$$

100 Ohm Resistor:

$$I_2 = 125 / 100 = 1.25\text{A}$$

50 Ohm Resistor:

$$I_3 = 125 / 50 = 2.5\text{A}$$

$$4. \quad V_1 = V_2 = V_3 = 125\text{V}$$

$$5. \quad \text{Use Watt's law } P = V * I$$

20 Ohm Resistor:

$$P_1 = 125\text{V} * 6.25\text{A} =$$

$$781.25\text{W}$$

100 Ohm Resistor:

$$P_2 = 125\text{V} * 1.25\text{A} =$$

$$156.25\text{W}$$

50 Ohm Resistor:

$$P_3 = 125\text{V} * 2.5\text{A} =$$

$$312.5\text{W}$$